

High-Voltage, Low-Threshold, Low-power Voltage Detector

**for Energy Harvesting, Internet of Things,
RF Power Transfer, and Event-Driven Sensing**


Zero-Power Monitoring and Wake-Up for Energy Harvesting, Wireless Sensors, and Remote-Controlled Devices

Plamen Proynov

5 April 2017




Typical energy harvesting system

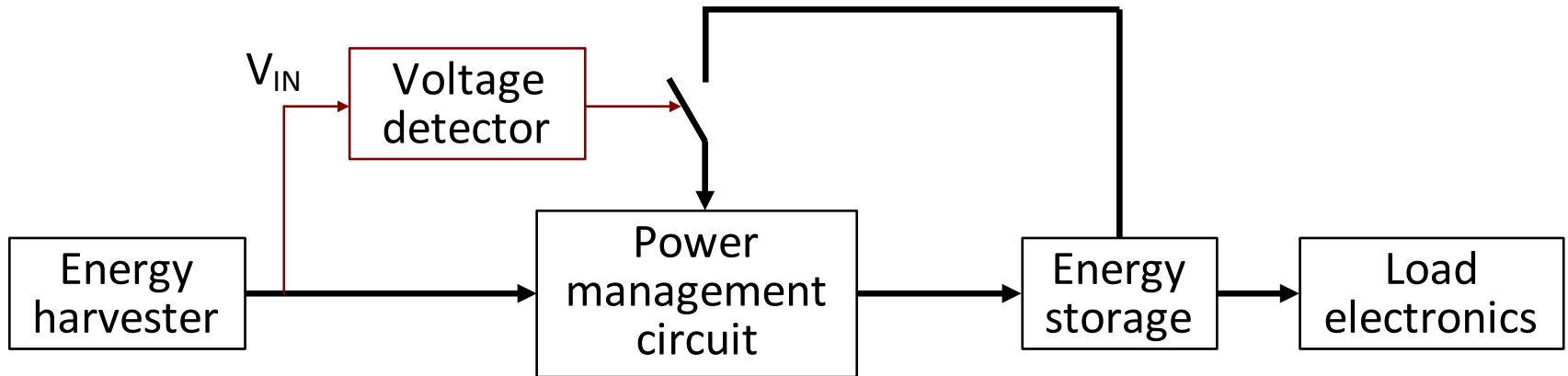


Inefficient with realistic sources
e.g. body-worn 2.4GHz rectenna:

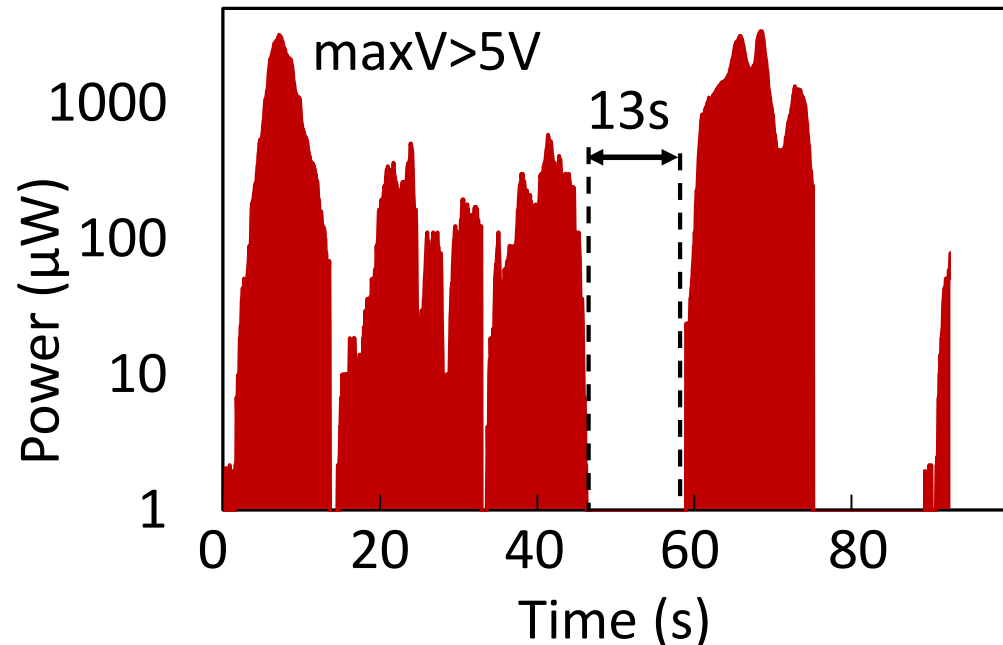- Highly dynamic power
- Long gaps between pulses of energy




Ferroelectret energy harvester

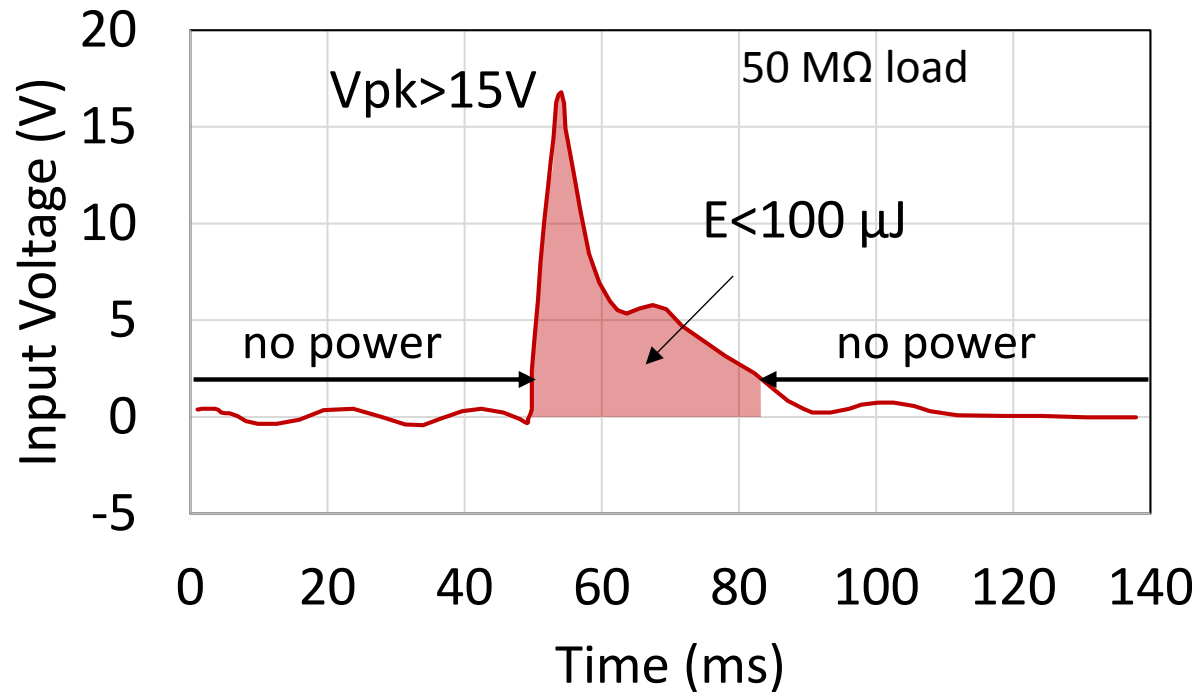

Peak power: 6 μ W

Source resistance: >50 M Ω

Pulse width (V>0.5V): 36 ms

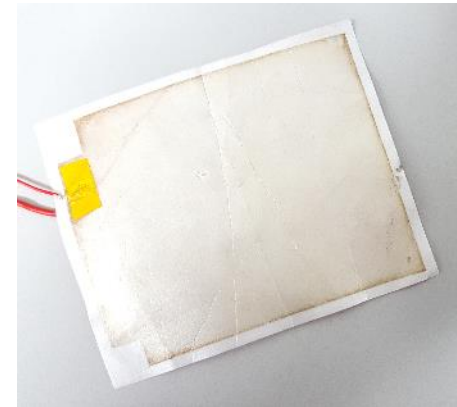

Problematic features:

- Mostly gaps
- High voltage could damage electronics
- No current

Requirements for the voltage detector:

- Withstand high voltages (up to 20V)
- Low threshold
- Low source loading
- Low quiescent consumption

Commercially available options


- Comparators – require continuous power supply, e.g. TS881:
Minimum supply voltage $V_{CC} = 0.85V$
Input bias current $I_{IB} < 10 \text{ pA}$
Supply current $I_{CC} = 210 \text{ nA}$ (at $1.2V V_{CC}$)
- Voltage detectors – input powered

	ON threshold (V)	Max input voltage (V)	Input current @ $V_{IN} < V_{TH}$ (nA)	Input current @ $V_{IN} > V_{TH}$ (nA)	Output leakage (nA)	Max output voltage (V)
ZSPM4121	1.7	5.5	0.1	40	100	-
TS12001	0.78	2.5	0.1	590	20	-
XC6120	1	6	-	350	1	7
UB20M	0.6	20	0.03	0.013	<0.1	5.5

Low ON threshold leads to low maximum input voltage

UB20M: lowest threshold, highest max input voalteg


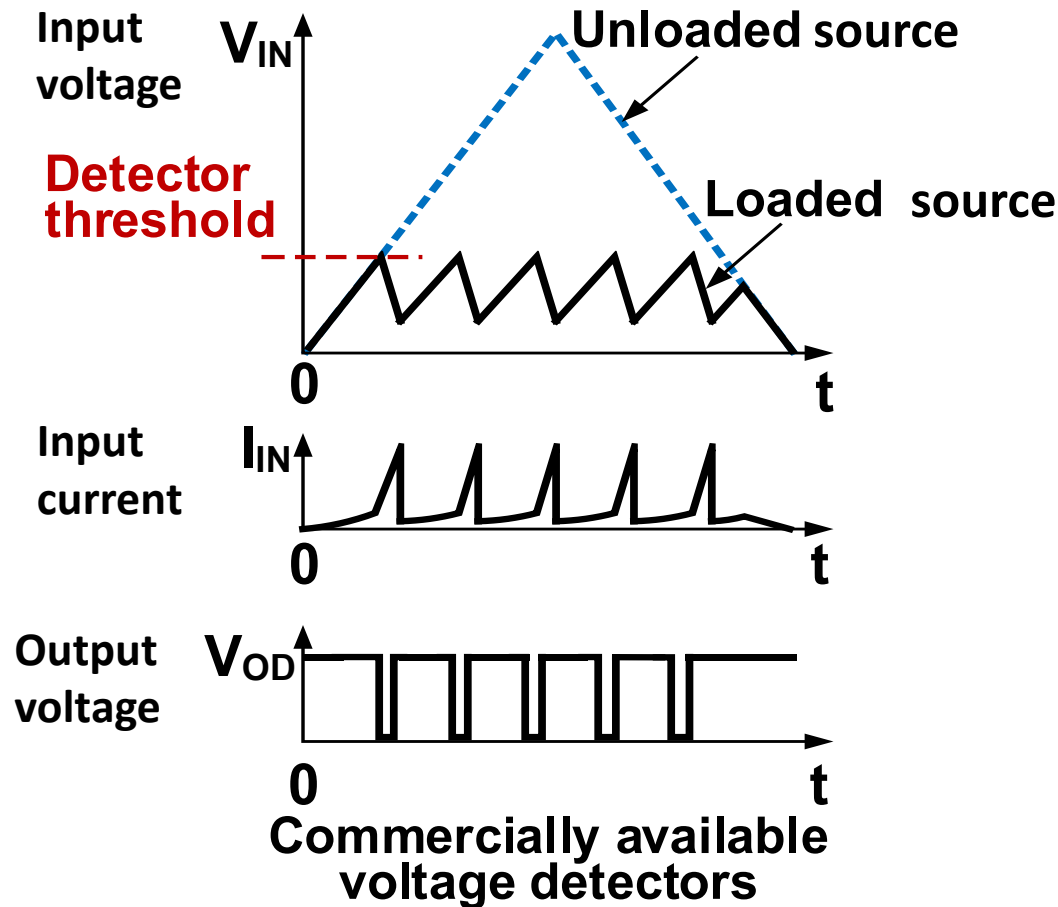
Operation of a commercially available voltage detector with the ferroelectret source



- Input is clamped
- Oscillations on the output


UB20M Voltage detector (SOT23-5)

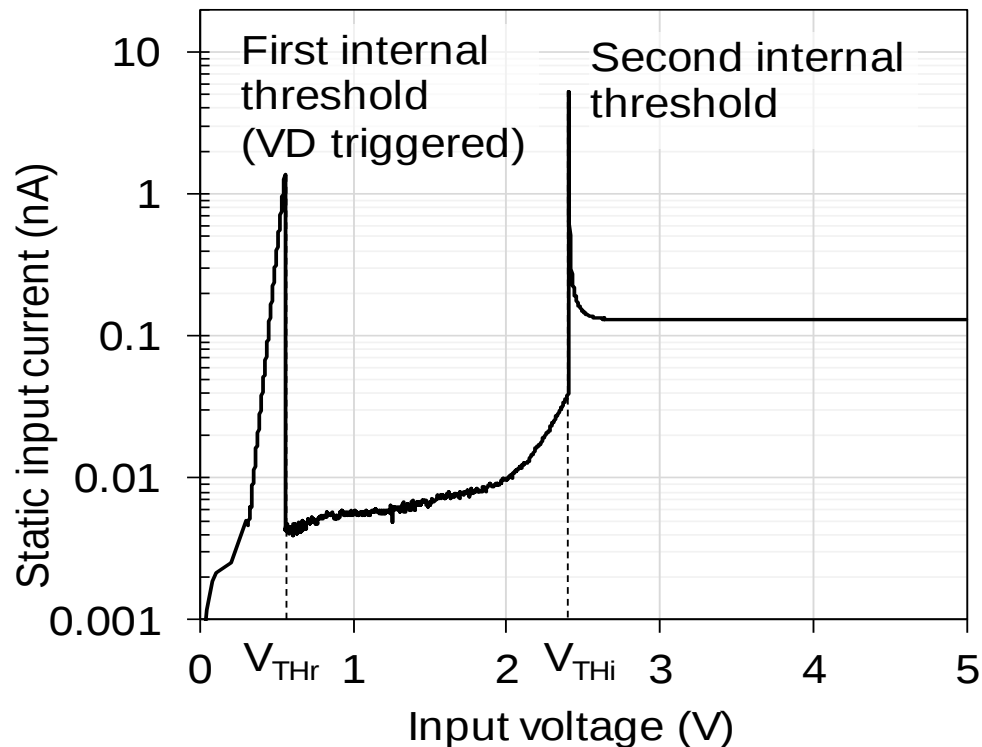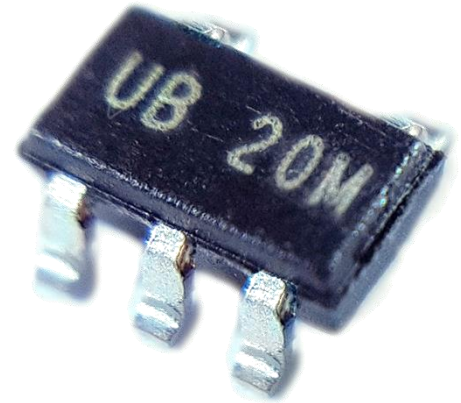- Threshold voltage: 600mV
- Maximum input voltage: up to 20V
- Output leakage: below 100pA
- Power consumption: 5.4pA at 1V
- Peak static input current at turn-on: 1.5 nA




UB20M Voltage detector



- Effect of dV_{in}/dt :

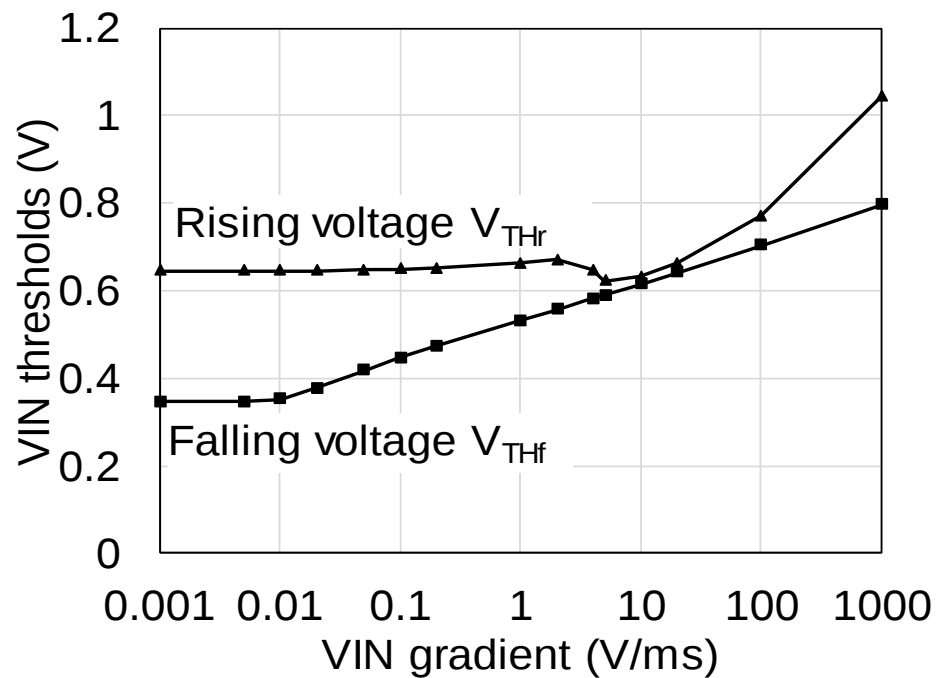


- Temperature effects:

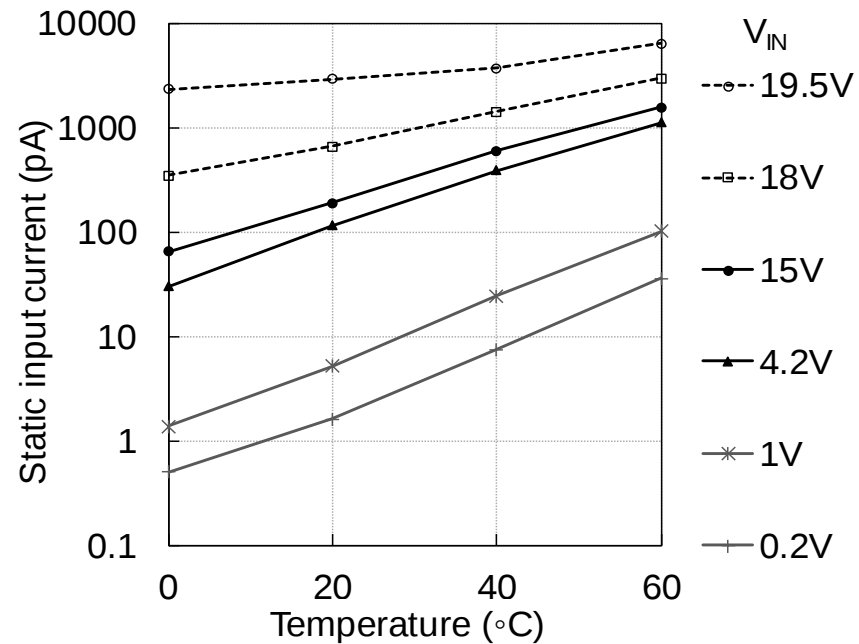

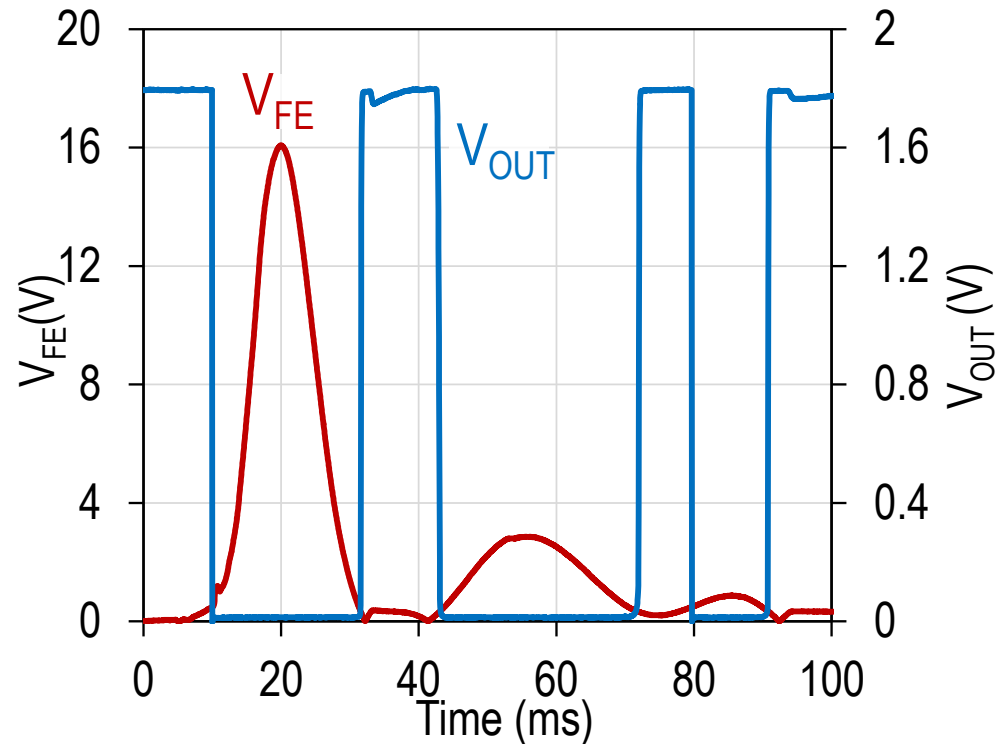
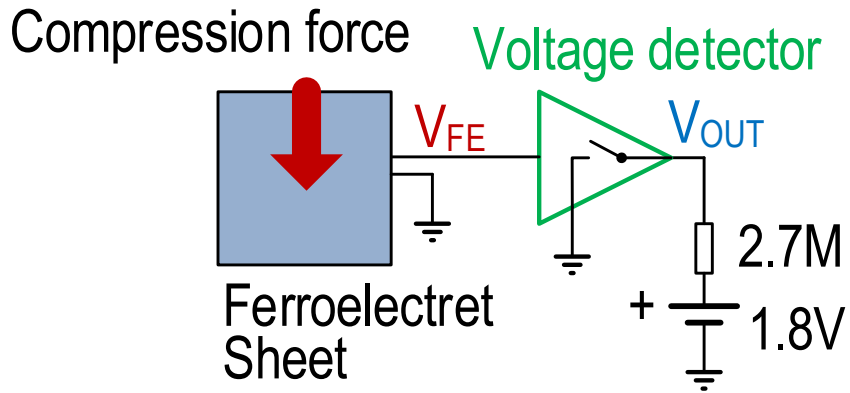
Captured waveform with the ferroelectret harvester



Passive RF wake-up

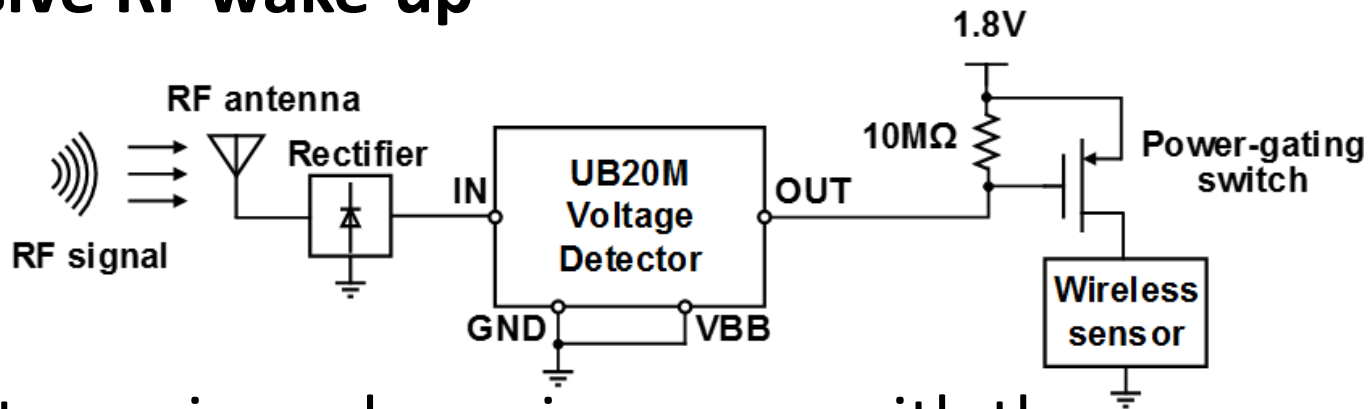

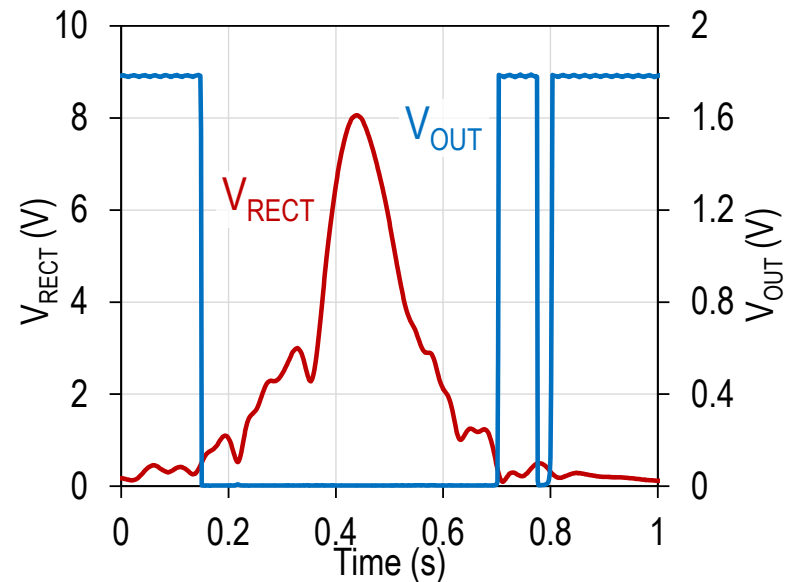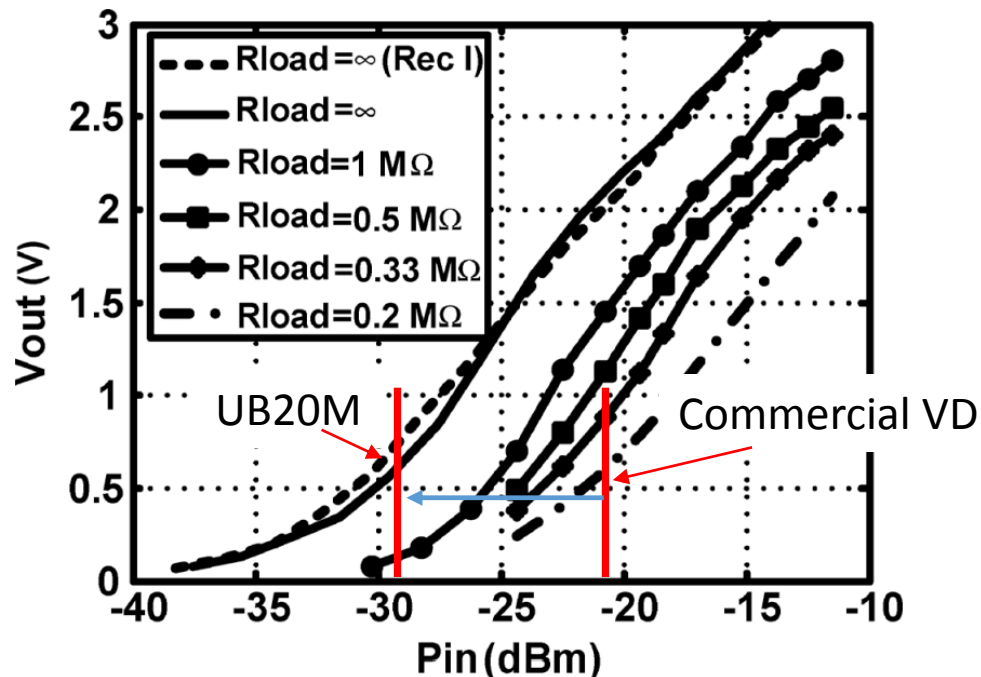
- Rectenna impedance increases with the distance, from $1\text{k}\Omega$ up to $\text{G}\Omega$



Rectenna output voltage as a function of the RF input power for different loads
source: Stoopman *et al.*, 2014

Other applications


Oscillator:

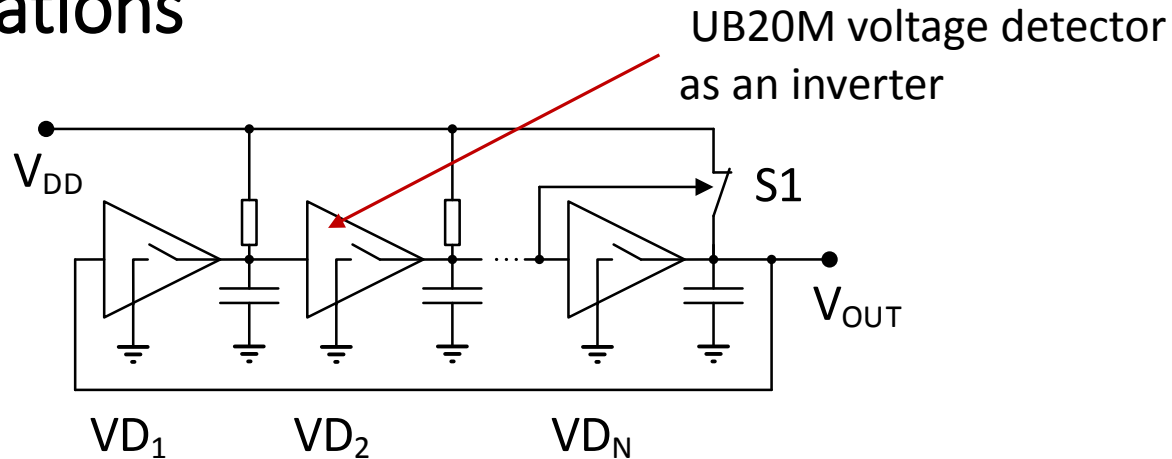

VD as an inverter – n-stage ring oscillator:


- Low power – 35nA at 1.1V
- Low duty cycle – 1.7%
- Frequency - 180 Hz

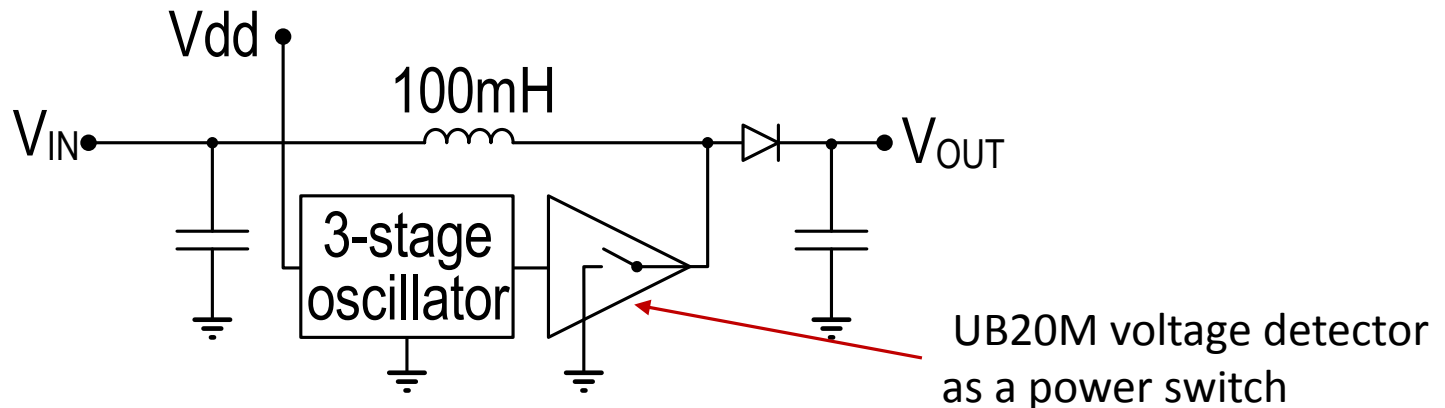Application – gate driving for a low-power boost converter for high sensitivity RF monitoring and wake-up (-36 dBm / 250 nW)




Power path control in energy harvesting systems with storage

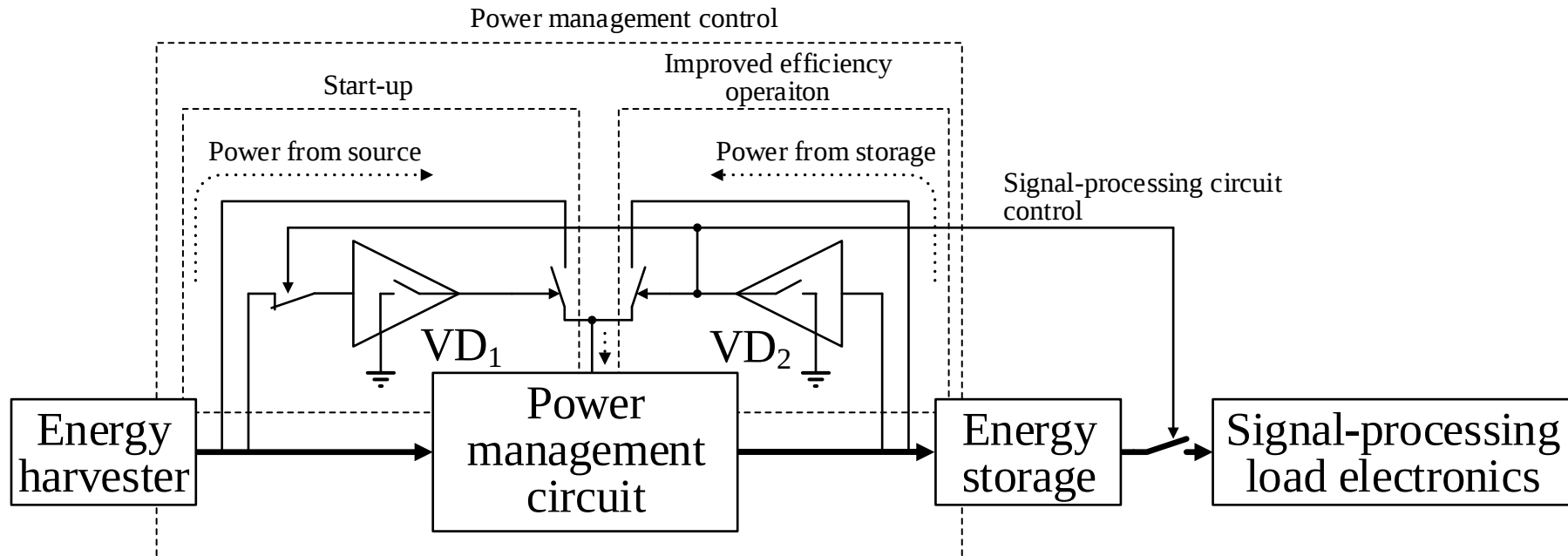- Power management can be powered from two sources:
 - Energy harvester during start-up ($V_{IN} > 450\text{mV}$, $V_{STORAGE} < 600\text{mV}$)
 - Energy storage when sufficient voltage is reached ($V_{STORAGE} > 600\text{mV}$)




Other high impedance sources


- Piezoelectric PVDF strips

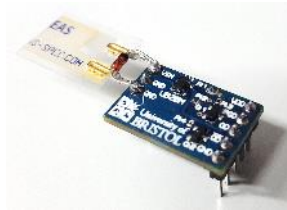

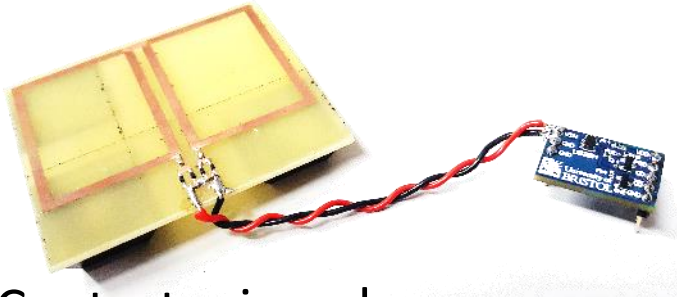- 2G, Sigfox, RF Rectenna for passive wake-up




- Contact microphone

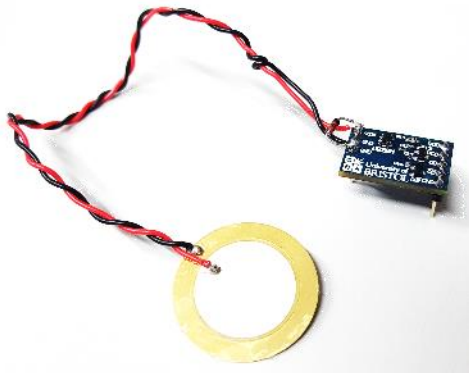

We are considering also:

- Infra-red receiver
- Ultrasound receiver
- Thermopile

Demos

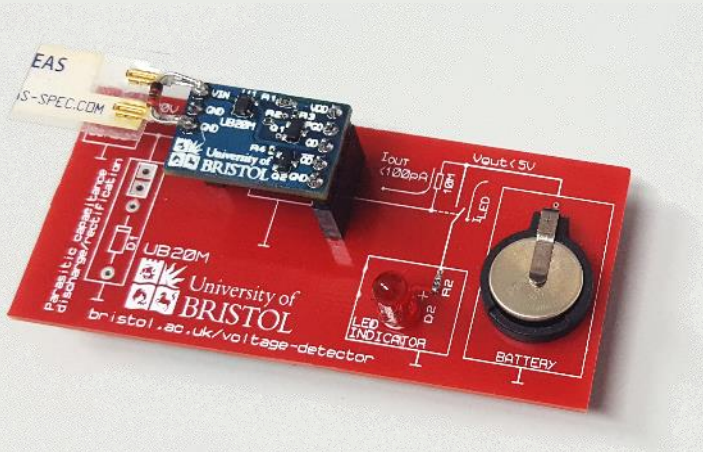

Team

Chunhong Zhang,
Guang Yang,
Salah Adami,
Bernard Stark

Website and free samples

bristol.ac.uk/voltage-detector

Questions?